

TABLE OF CONTENTS

PREFACE	xvii
Part 1 BASIC CONCEPTS.....	1
1 Electronic Concepts.....	3
Current	3
Charge	5
Voltage.....	6
Direct and Alternating Voltage and Current	8
Harmonics	11
Measurement of AC Voltage or Current	12
Frequency, Rise/Fall Times, and Period	13
Frequency Measurement	16
Complex Waveforms (Fourier Analyses).....	18
Chapter Endnotes	23
Direction of Current Flow	23
Some Standard Symbols Used in Electronics	24
Some Fundamental Definitions.....	25
Important Names in Electronics.....	26
2 Propagation Times.....	27
Propagation Speed.....	27
Propagation Times	28
Trace Configurations and Signal Propagation.....	29
Circuit Timing Issues	32
Wavelength	35

3 Electrical Components	37
The Three Basics	37
Resistance	38
Ohm's Law	39
Capacitance	43
Charge Storage	47
Formula for Capacitance	48
Capacitance Functions and Effects	49
Inductance	50
Formulas for Inductance	55
Charge and Discharge Currents	56
Resonance	60
4 Voltage and Current Changes and Time Constants.....	63
Voltage and Current Changes Through Resistors	63
Voltage and Current Changes Through Capacitors	64
Voltage and Current Changes Through Inductors	66
Some Interesting Inductive Circuit Dynamics	69
Time Constants	71
A Note on Charge and Discharge Equations	76
5 Resistance	77
Kirchhoff's Laws	77
Series Resistors	79
Parallel Resistors	81
Voltage Dividers	83
Amplifier Feedback and Gain	85
Power	86
Equivalent Circuits	88
Power Curve	91
Power Sources	93
Conductance	94
6 Reactance	97
Capacitive Reactance	98
Inductive Reactance	99
Ohm's Law for Reactance	101
Series LC Combinations	104
Parallel LC Circuits	107
Resonance	111
Poles and Zeros	115

Susceptance 119

7 Impedance and Phase Shift..... 121

 Impedance 121

 Effect of Frequency 128

 Another RC Example 129

 Classic RC Filter 131

 Combining Impedances 133

 Resonance and Q 134

 Series RLC Circuits 137

 Series RLC at Resonance 140

 Admittance 142

 Chapter Endnotes 144

 Detailed Calculations for Figure 7-8 144

 RLC Simulation 145

 Imaginary Numbers 146

Part 2 SIGNAL INTEGRITY ISSUES..... 147

8 Signal Integrity Overview 149

9 Electromagnetic Interference (EMI) 155

 Background 155

 Fields and Cancellations 156

 Some Basic Truths 158

 Signal Coupling 159

 Loop Area 161

 Slots in Planes 1 162

 Return Pathways 163

 Power Plane Returns 164

 Changing Trace Layers 165

 Unrelated Planes 166

 Stripline 167

 Stubs 168

 Common Mode 169

 The 20-H Rule 173

 Picket Fences (Faraday Shields) 174

10 Reflections and Transmission Lines	175
Communications Model	175
Transmission Lines	178
Critical Length	181
Reflection Coefficients.....	183
Visualizing Reflections	184
Determining Trace Impedance	185
Termination Techniques.....	190
Parallel	192
Thevenin	192
AC Termination	194
Series.....	194
Diode.....	195
Some Design Issues.....	196
Changing Trace Layers 1	196
Power Planes.....	197
Changing Trace Layers 2	197
Slots in Planes 2	199
Stubs.....	200
Absolute vs. Relative Value of Z_0	201
Chapter Endnote.....	203
On Formulas.....	203
11 Some Transmission Line Simulations.....	207
Basic Simulation	207
Series Termination	215
Placement Issues	217
Branches, or Ys.....	219
12 Crosstalk.....	221
Forward versus Backward Crosstalk	221
Backward Crosstalk	223
Forward Crosstalk	225
In Summary.....	226
Estimating Crosstalk	226
Calculations.....	226
Coupling.....	227
Distance	227
Terminations	229
UltraCAD Calculator	230
HyperLynx Simulation Tool	231
Design Considerations	232

Slots in Planes 3	232
Guard Bands.....	233
13 Crosstalk Simulations	235
Basic Model	235
Add an Uncoupled Region	239
Effect of Length	240
Stripline.....	242
Stripline With Terminations.....	242
More Realistic Example	244
Summary	247
14 Differential Traces and Impedance.....	249
Background	249
Advantages.....	249
Key Assumptions	251
Design Rules	255
Design Rule 1 (Equal Length).....	255
Common Mode Implications	255
Differential Signals and Loop Areas.....	256
Design Rule 2 (Close Together).....	257
Rule 2 Consequence.....	258
Design Rule 3 (Differential Impedance)	260
Differential Mode Impedance	260
Common Mode Impedance.....	261
Design Rule 4 (Constant Separation)	262
Differential Simulations	262
Calculating Differential Impedance	265
Edge Coupled.....	266
Broadside Coupled.....	268
15 Bypass Caps and Decoupling Systems	269
Traditional Approach	269
Size and Quantity	273
Placement.....	275
Connection	276
Power System Impedance Approach.....	277
Ideal Response	277
Capacitor Response.....	278
Inductance Effects.....	278
Multiple Capacitors.....	280
Additional Capacitor Value.....	281

Planar Capacitance.....	282
Equivalent Series Resistance (ESR).....	285
Self Resonant Frequencies.....	287
Effects of Multiple Capacitors.....	288
Parallel Capacitors.....	288
Resonance.....	290
Impedance at Self-Resonant Frequency.....	291
Impedance at Anti-Resonance.....	292
General Case Analysis.....	293
Consequences.....	294
Summary.....	296
16 Power Systems.....	297
Power Supply Voltages.....	297
Need For Power Planes.....	300
Strategies For Designing With Plane.....	300
Some Design Rules.....	303
Connecting Reference Planes Together.....	303
Overlapping Planes.....	304
Decoupling to Wrong Plane.....	305
Signals Crossing Separations.....	305
Stack-Ups.....	307
Conclusion.....	308
17 Lossy Lines and Eye Diagrams.....	311
Lossy Lines.....	311
Skin Effect.....	312
Dielectric Absorption.....	314
Lossy Line Model.....	314
Eye Diagrams.....	316
Equalization.....	318
Passive Equalization.....	319
Active Equalization.....	319
Summary.....	320
Part 3 Appendices, Glossary, and Index.....	323
Appendices.....	325
A UltraCAD's Square Wave Simulator.....	325
B Why Inductors Induct.....	329
C Logarithms.....	345

Table of Contents**xv**

D Phase Shift Simulation	351
E Complex Algebra	357
F Transmission Line Simulation.....	367
G Echo Illustration	369
H UltraCAD Freeware Calculators	371
I TDRs and VNAs	375
J Right Angle Corners.....	383
Glossary.....	387
Index	397
About the Author.....	401